

200MHz TWC: 628MHz-  
coupler improvement


# Content




- More work on 628-coupler improvement
- What is limiting the current 628MHz-coupler?
- General overview/ insight
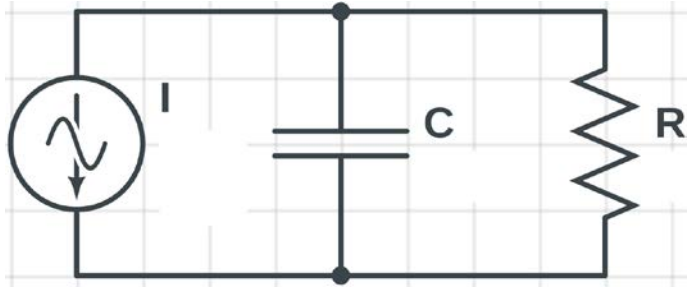
# Circuit model of coupler for 628MHz-mode

- Approximation of cavity & coupler with equivalent generator circuit
  - Only for 628MHz mode and very simplified



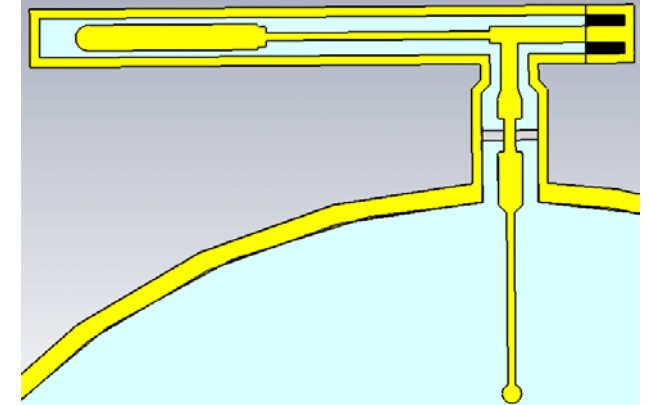C: probe capacitance  
I: displacement current  
R: load




- Power extracted from HOM:

$$P = \frac{1}{2} I_0^2 \operatorname{Re}\{Z\} = \frac{1}{2} I_0^2 * \frac{1/R}{(1/R)^2 + (\omega C)^2}$$


- > raise induced current I
- > compensate probe capacitance C
- > decrease load R

# Compensation of probe capacitance



- Place an inductance for compensation

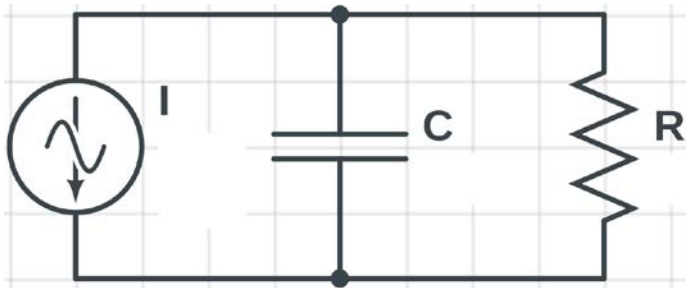
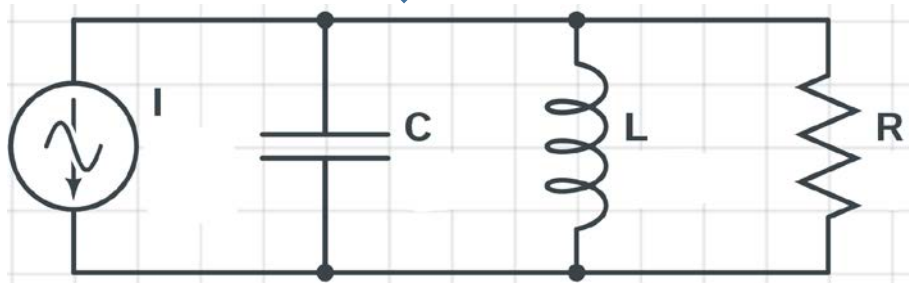
$$P = \frac{1}{2} I_0^2 \operatorname{Re}\{Z\} = \frac{1}{2} I_0^2 * \frac{1/R}{(1/R)^2 + (\omega C)^2}$$






L: compensating inductance

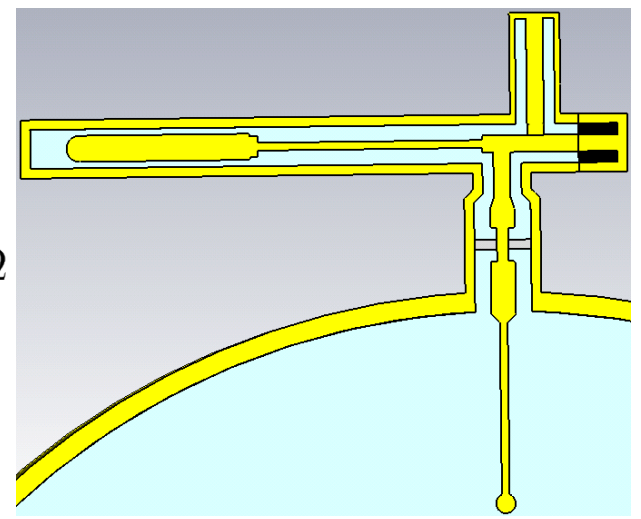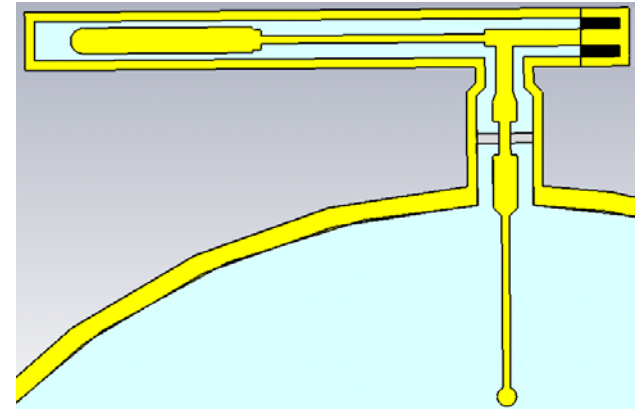

$$+j\omega L = +j38\Omega @628\text{MHz}$$
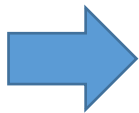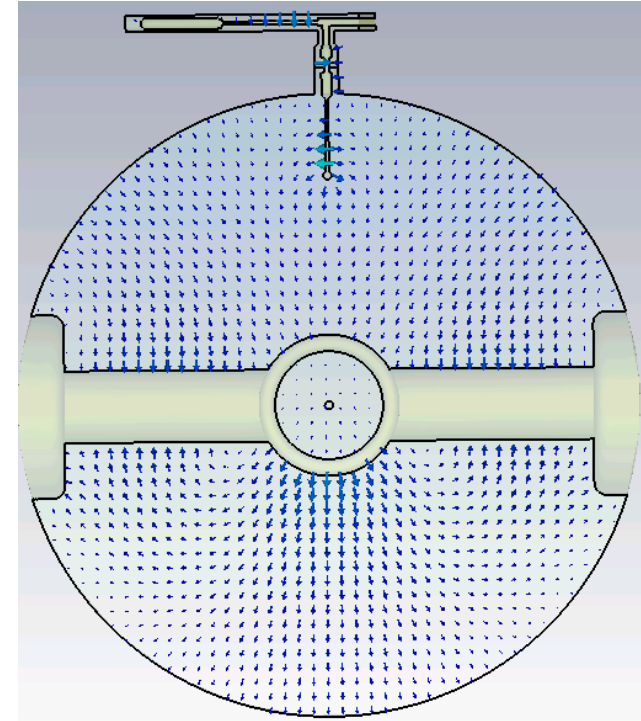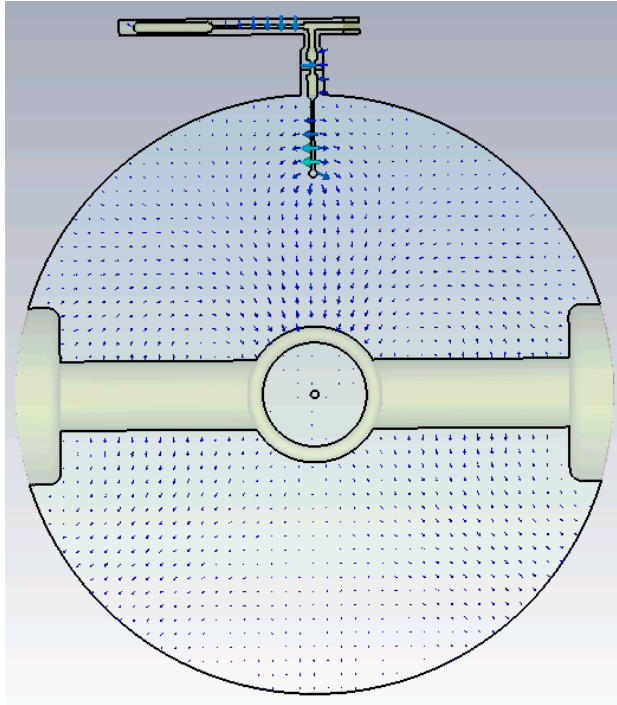
# Compensation of probe capacitance

- Evaluate performance with the two 628MHz degenerate modes



Damping one mode increases the other of the two degenerate modes!



# Compensation of probe capacitance


- Single-cell simulations

Present coupler				Compensated coupler			
f [MHz]	Q	R/Q [ $\Omega$ ]	R [k $\Omega$ ]	f [MHz]	Q	R/Q [ $\Omega$ ]	R [k $\Omega$ ]
624.5	57	2.6	0.15	625.9	331	6.4	2.13
629.1	755	5.9	4.4	629.7	964	2.7	2.6



Decrease of a factor 1.7
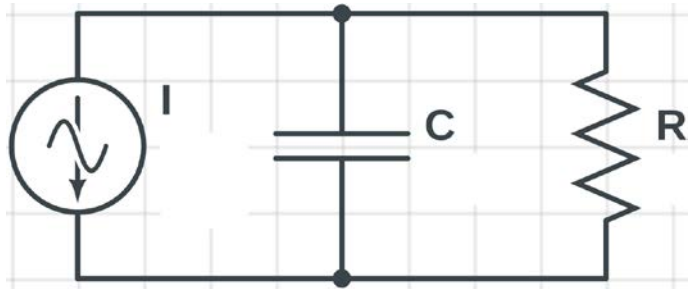
# Reduction of load impedance


- Use of a  $\lambda/4$ -transformer (narrowband)


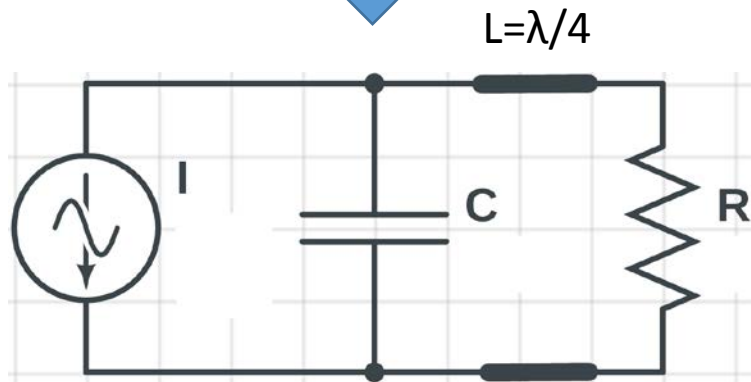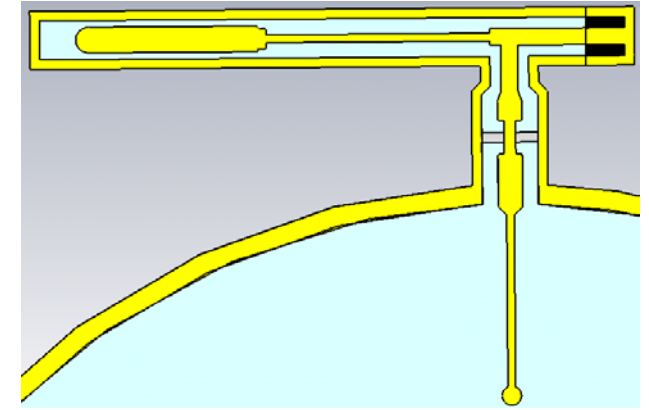
$$P = \frac{1}{2} I_0^2 \operatorname{Re}\{Z\} = \frac{1}{2} I_0^2 * \frac{1/R}{(1/R)^2 + (\omega C)^2}$$



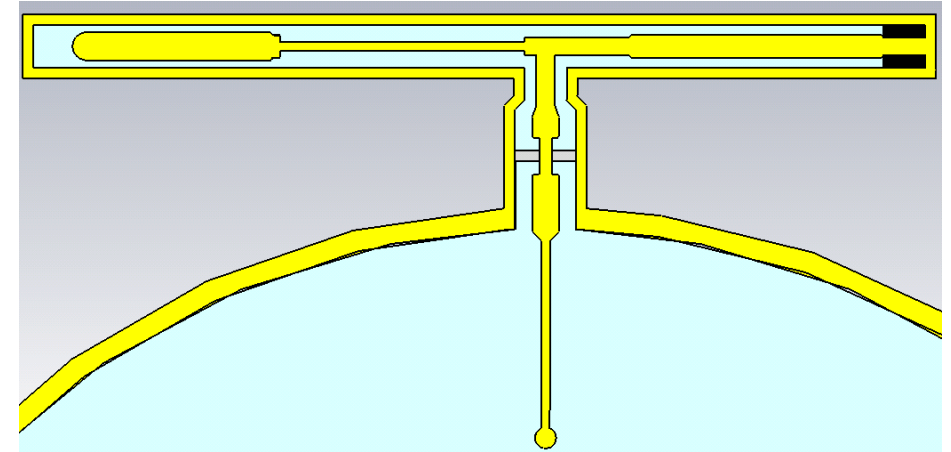Effective load:  
30  $\Omega$   
@628MHz





# Reduction of load impedance

- Single-cell simulations

Present coupler				Narrowband coupler			
f [MHz]	Q	R/Q [ $\Omega$ ]	R [k $\Omega$ ]	f [MHz]	Q	R/Q [ $\Omega$ ]	R [k $\Omega$ ]
624.5	57	2.6	0.15	626.8	210	6.4	1.33
629.1	755	5.9	4.4	629.8	522	2.8	1.46

Decrease of a factor 3.0





# Outlook

- Combination of the improvements not easy
- Generator approach made is too simplified
- Model the cavity as a lumped resonance circuit